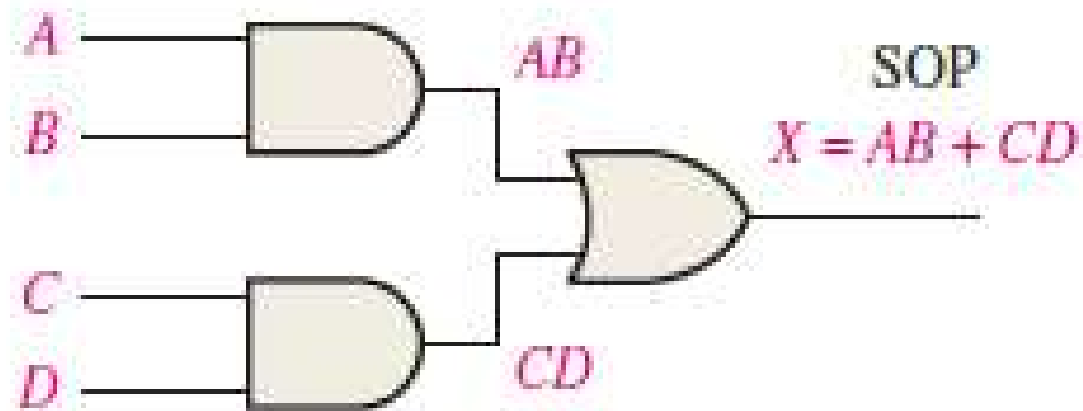


Combinational Circuits

AND-OR Logic

- Figure shows an AND-OR circuit consisting of two 2-input AND gates and one 2-input OR gate



AND-OR Logic


- The truth table for a 4-input AND-OR logic circuit is shown in the Table below.
- The intermediate AND gate outputs (the *AB* and *CD* columns) are also shown in the table.

Inputs						Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>AB</i>	<i>CD</i>	<i>X</i>
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	1	1
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	0	0	0
0	1	1	1	0	1	1
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	0	0	0
1	0	1	1	0	1	1
1	1	0	0	1	0	1
1	1	0	1	1	0	1
1	1	1	0	1	0	1
1	1	1	1	1	1	1

AND-OR-Invert Logic


- When the output of an AND-OR circuit is complemented (inverted), it results in an AND-OR-Invert circuit.
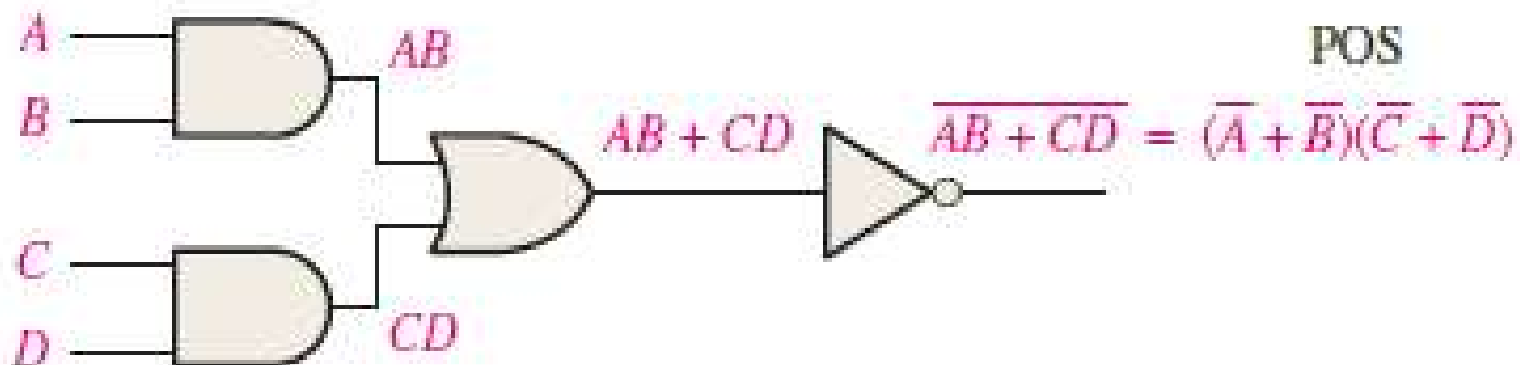
$$X = (\bar{A} + \bar{B})(\bar{C} + \bar{D}) = (\overline{AB})(\overline{CD}) = \overline{\overline{\overline{AB}}(\overline{\overline{\overline{CD}}})} = \overline{\overline{AB} + \overline{\overline{\overline{CD}}}} = \overline{\overline{AB} + CD} = \overline{AB} + \overline{CD}$$





Exclusive-OR Logic

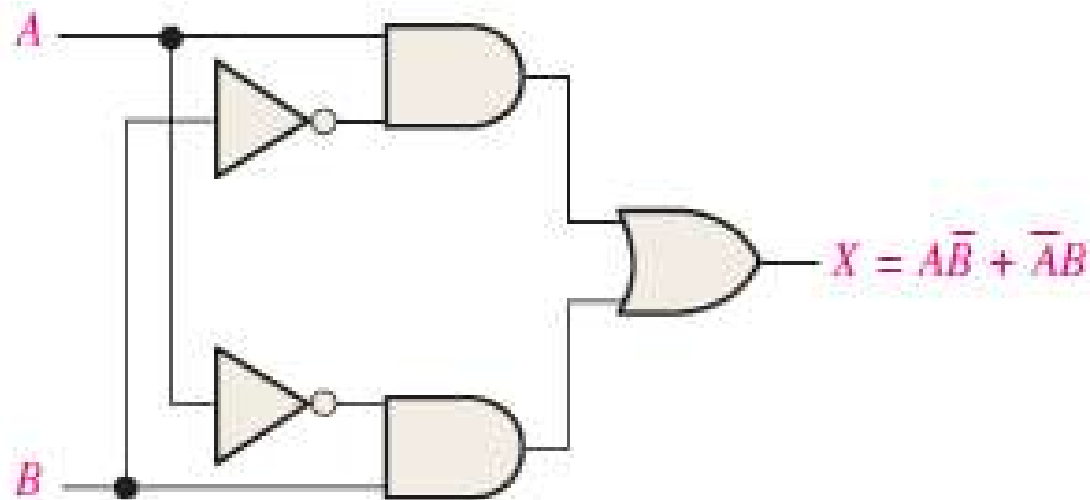- Although this circuit is considered a type of logic gate with its own unique symbol, it is actually a combination of two AND gates, one OR gate, and two inverters, as shown below



From a Boolean Expression to a Logic Circuit

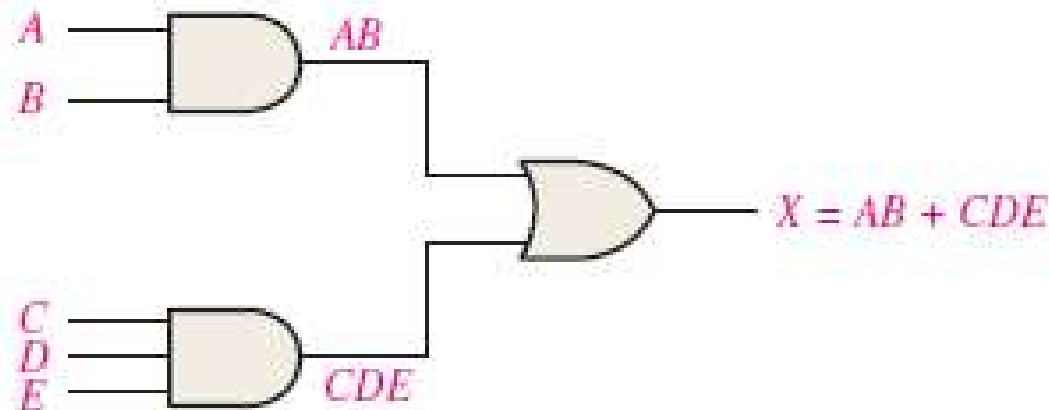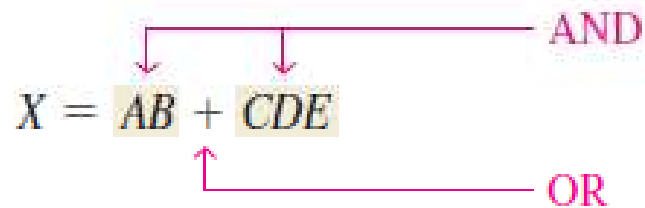- Let's examine the following Boolean expression: $X = AB + CDE$




From a Boolean Expression to a Logic Circuit

- let's implement the following expression:

$$X = AB(C\overline{D} + EF)$$

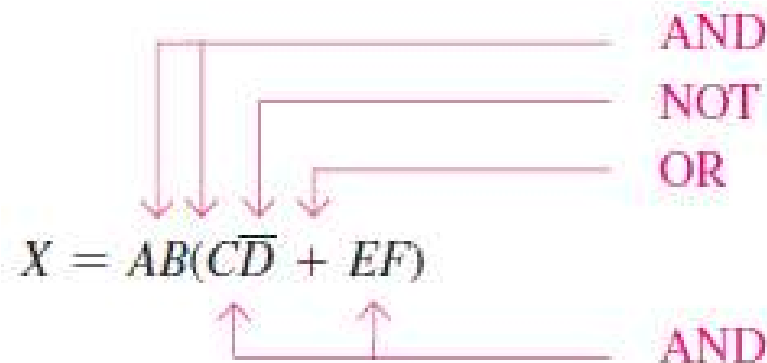- A breakdown of this expression shows that the terms AB and $(C\overline{D} + EF)$ are ANDed.
- The term $(C\overline{D} + EF)$ is formed by first ANDing C and \overline{D} and ANDing E and F , and the Oring these two terms.



From a Boolean Expression to a Logic Circuit


- Before you can implement the final expression, you must create the sum term $(C \overline{D} + EF)$ but before you can get this term; you must create the product terms $C\overline{D}$ and EF ;
- but before you can get the term $C\overline{D}$ *you must create \overline{D} .*
- The logic gates required to implement

$$X = AB(C\overline{D} + EF)$$

are as follows

From a Boolean Expression to a Logic Circuit

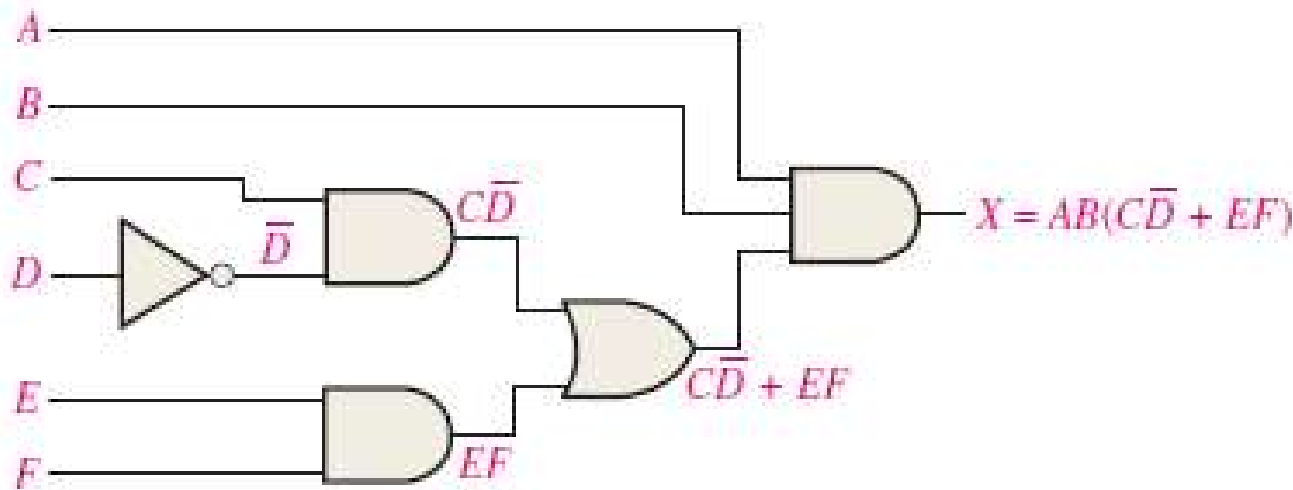- One inverter to form \overline{D}
- Two 2-input AND gates to form $C\overline{D}$ and EF
- One 2-input OR gate to form $(C\overline{D} + EF)$
- One 3-input AND gate to form X




From a Boolean Expression to a Logic Circuit

- Notice that there is a maximum of four gates and an inverter between an input and output in this circuit (from input D to output).
- Often the total propagation delay time through a logic circuit is a major consideration.
- Propagation delays are additive, so the more gates or inverters between input and output, the greater the propagation delay time.

From a Boolean Expression to a Logic Circuit

- It is usually best to reduce a circuit to its SOP form in order to reduce the overall propagation delay time.
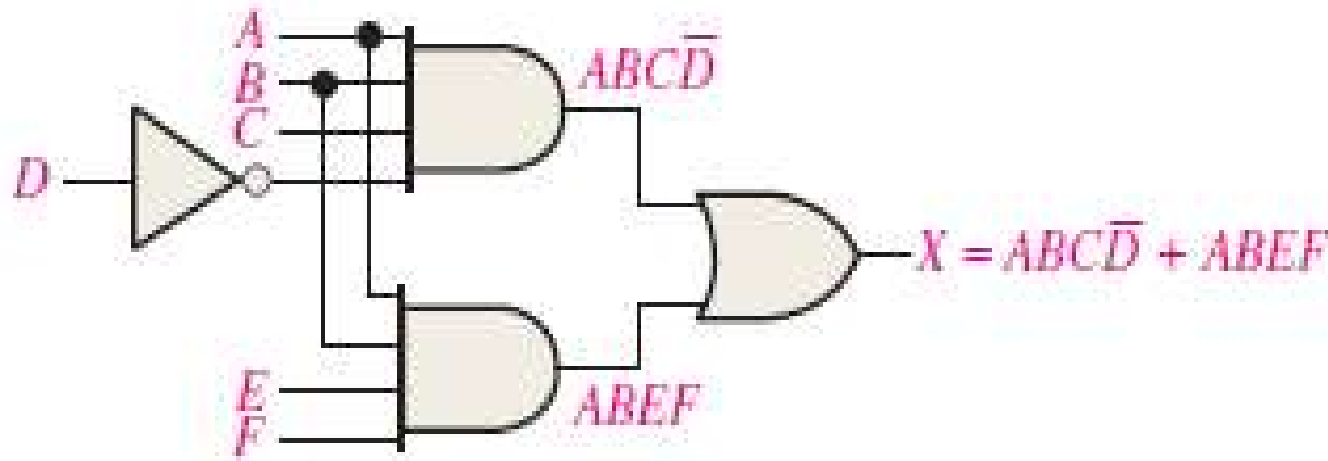
$$X = AB(C\bar{D} + EF) = ABC\bar{D} + ABEF$$




From a Truth Table to a Logic Circuit

- If you begin with a truth table instead of an expression, you can write the SOP expression from the truth table and then implement the logic circuit.

Inputs			Output	Product Term
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\overline{A}BC$
1	0	0	1	$A\overline{B}\overline{C}$
1	0	1	0	
1	1	0	0	
1	1	1	0	

From a Truth Table to a Logic Circuit

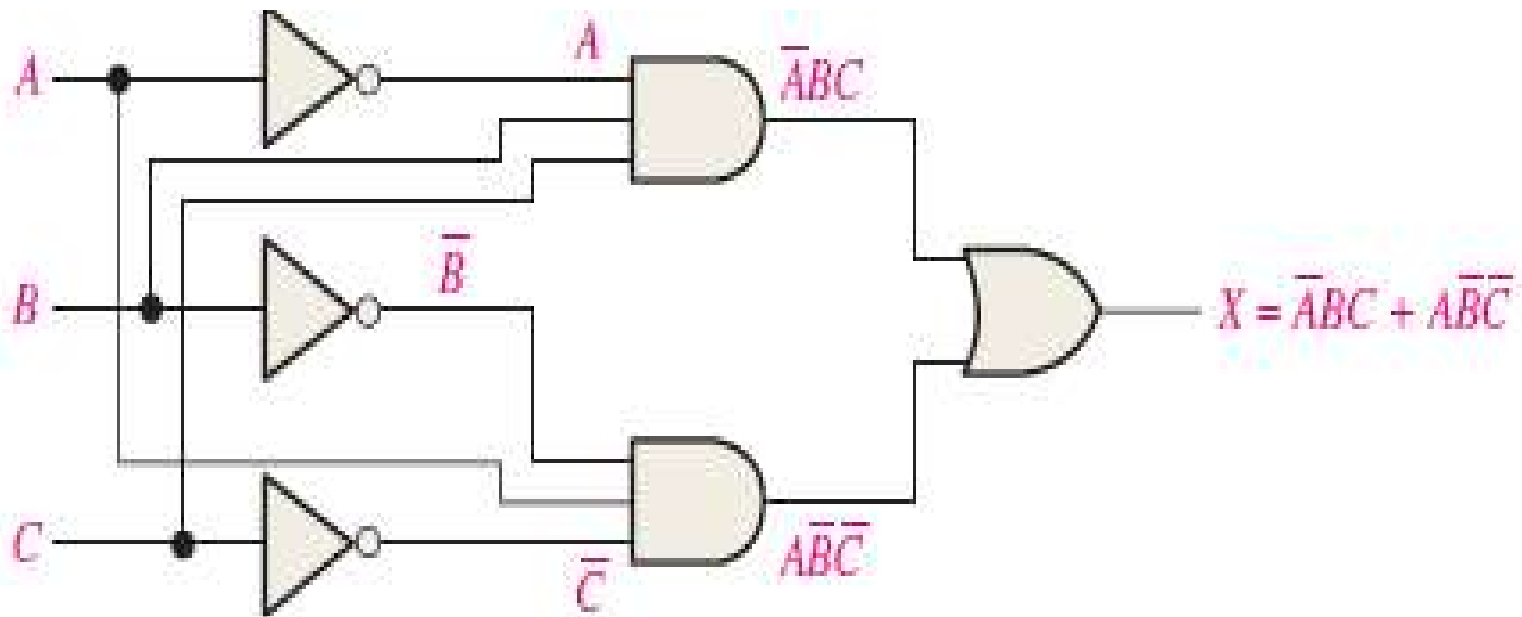- The Boolean SOP expression obtained from the truth table by ORing the product terms
- for which $X = 1$ is $X = \bar{A}BC + A\bar{B}\bar{C}$




From a Truth Table to a Logic Circuit

- Design a logic circuit to implement the operation specified in the truth table


Inputs			Output	Product Term
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\bar{A}BC$
1	0	0	0	
1	0	1	1	$A\bar{B}C$
1	1	0	1	$AB\bar{C}$
1	1	1	0	

From a Truth Table to a Logic Circuit

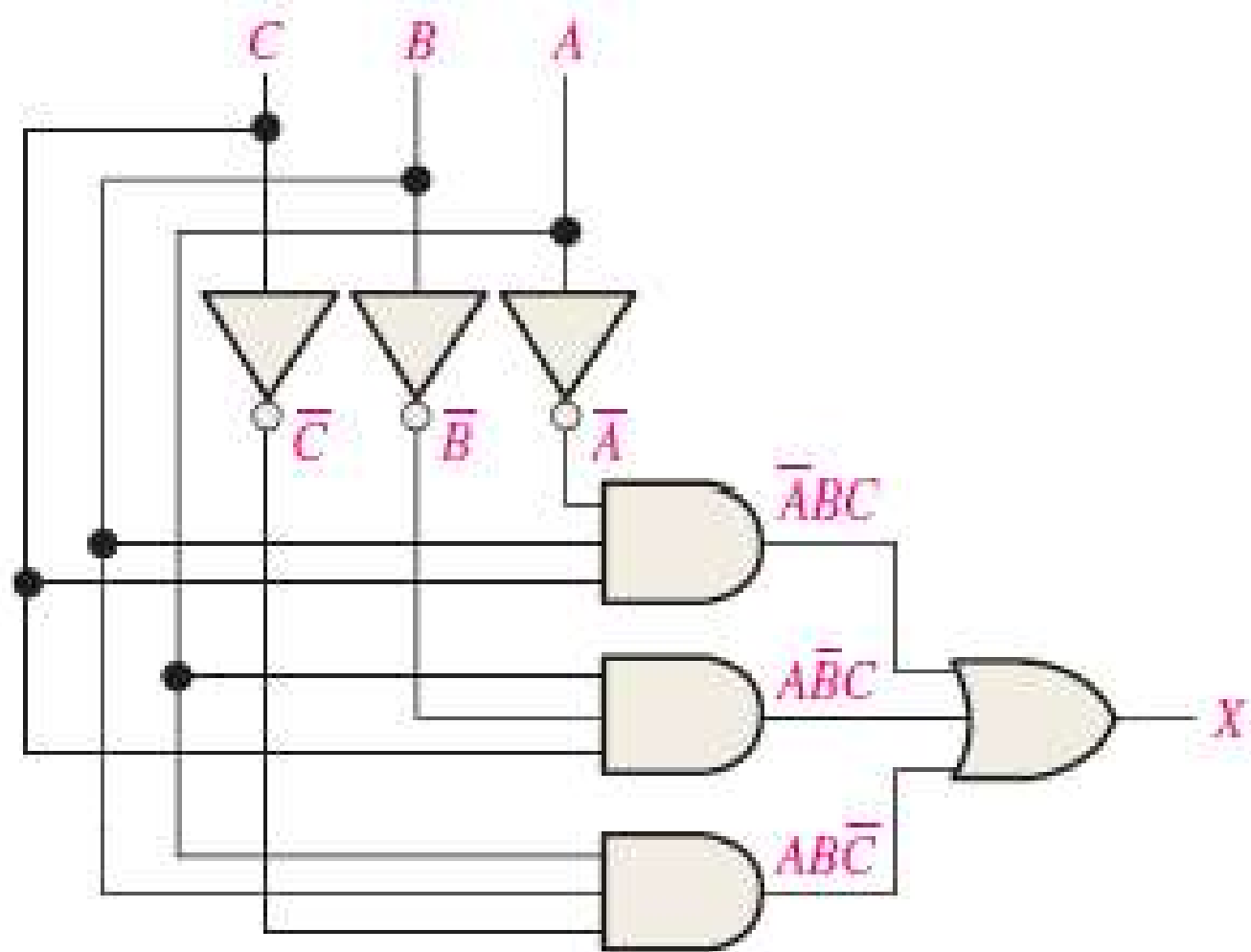- Notice that $X = 1$ for only three of the input conditions. Therefore, the logic expression is
$$X = \overline{A}BC + A\overline{B}C + AB\overline{C}$$
- The logic gates required are three inverters, three 3-input AND gates and one 3-input OR gate.



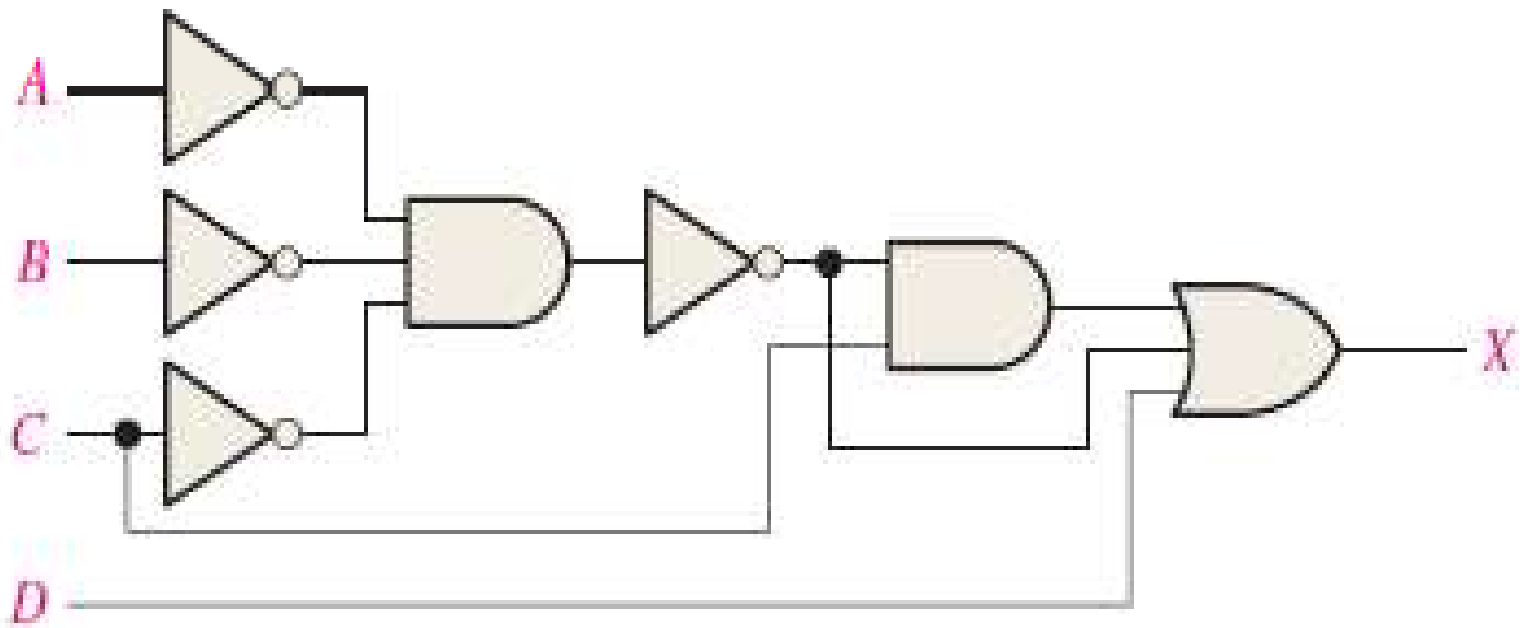- Reduce the combinational logic circuit in below to a minimum form.



Solution

The expression for the output of the circuit is

$$X = (\overline{\overline{A}\overline{B}\overline{C}})C + \overline{\overline{A}\overline{B}\overline{C}} + D$$

Applying DeMorgan's theorem and Boolean algebra,


$$\begin{aligned} X &= (\overline{\overline{A}} + \overline{\overline{B}} + \overline{\overline{C}})C + \overline{\overline{A}} + \overline{\overline{B}} + \overline{\overline{C}} + D \\ &= AC + BC + CC + A + B + C + D \\ &= AC + BC + C + A + B + \mathcal{C} + D \\ &= C(A + B + 1) + A + B + D \\ X &= A + B + C + D \end{aligned}$$

NAND Logic

$$\overline{AB} = \overline{A} + \overline{B}$$


NAND $\xrightarrow{\quad}$ \overline{AB} $\xleftarrow{\quad}$ negative-OR

$$\begin{aligned} X &= \overline{(\overline{AB})(\overline{CD})} \\ &= \overline{(\overline{A} + \overline{B})(\overline{C} + \overline{D})} \\ &= \overline{(\overline{A} + \overline{B})} + \overline{(\overline{C} + \overline{D})} \\ &= \overline{\overline{A}\overline{B}} + \overline{\overline{C}\overline{D}} \\ &= AB + CD \end{aligned}$$

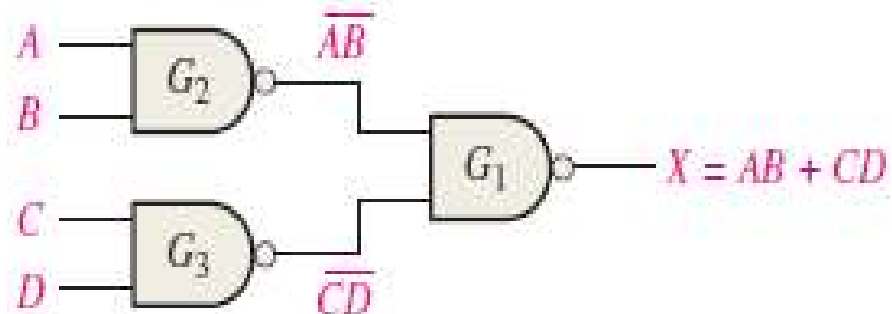


Try 1

- Determine the output (in terms of Boolean expressions) F.
- Complete the truth table for the function F.
- From the truth table, write the 'sum of products' expression for the function F

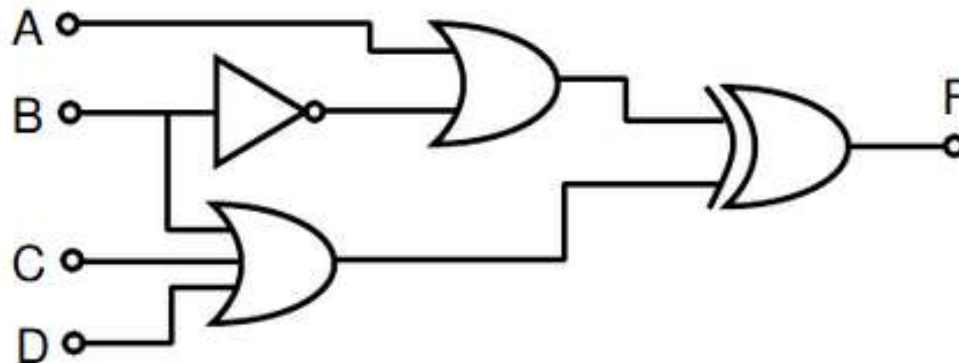


Try 2

- Determine the output F in the circuit shown
- By utilizing Boolean algebra, show that the function F obtained above is also equivalent to $(\overline{A} + B) \bullet (C + \overline{D})$

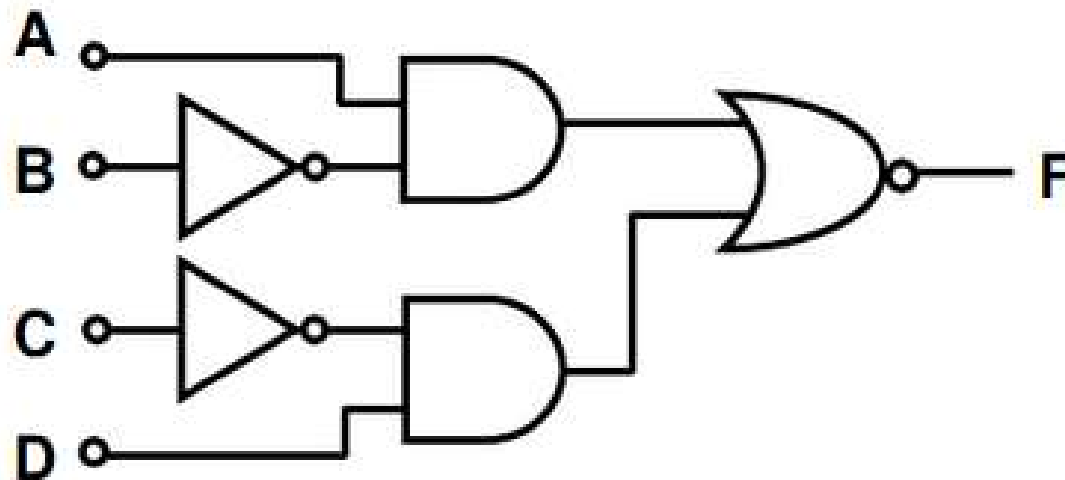


Try 3

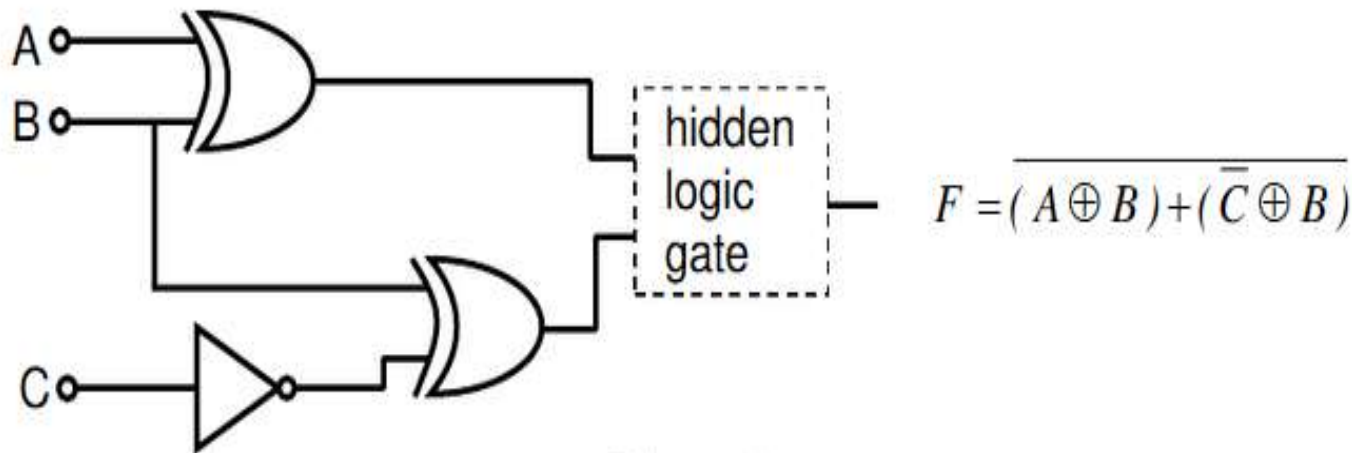- The circuit shown below in Figure 3 has a two-input logic gate hidden from view. By inspection of the output function F , identify the hidden logic gate
- Draw a truth table for the function F given in part (A) above.
- Derive an alternative 'sum of products' expression for F



The Half-Adder

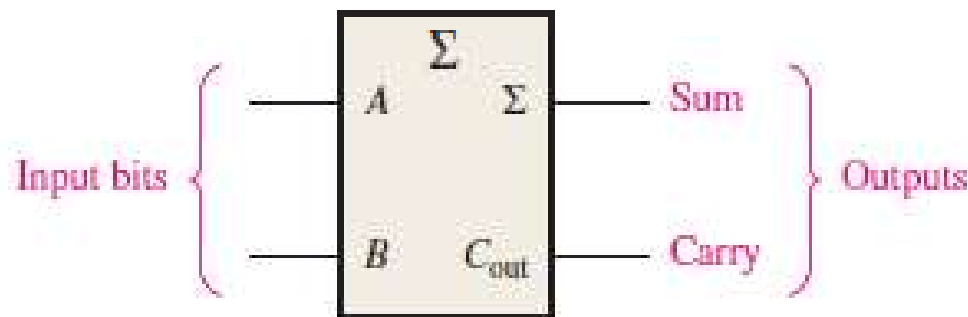- The half-adder accepts two binary digits on its inputs and produces two binary digits on its outputs—a sum bit and a carry bit.



The Half-Adder

Half-adder truth table.

A	B	C_{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Σ = sum

C_{out} = output carry

A and B = input variables (operands)

The Half-Adder


- Notice that the output carry (C_{out}) is a 1 only when both A and B are 1s; therefore, C_{out} can be expressed as the AND of the input variables.

$$C_{out} = A B$$

- Now observe that the sum output is a 1 only if the input variables, A and B , are not equal. The sum can therefore be expressed as the exclusive-OR of the input variables.


$$\Sigma = A \oplus B$$

The Half-Adder

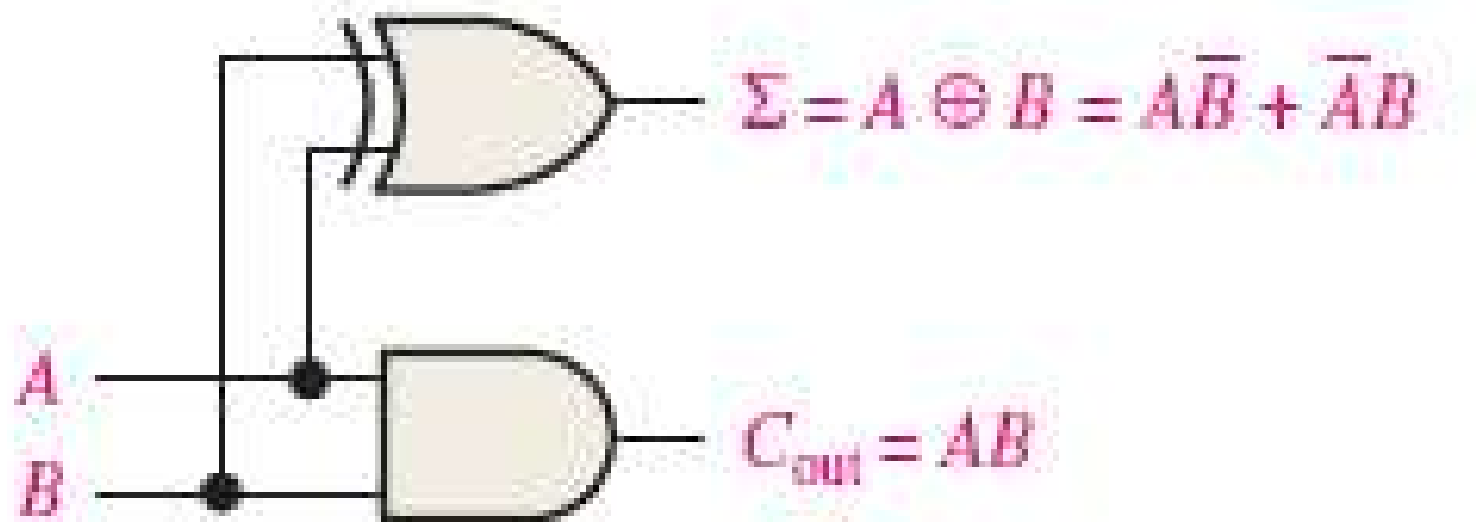

The Full-Adder

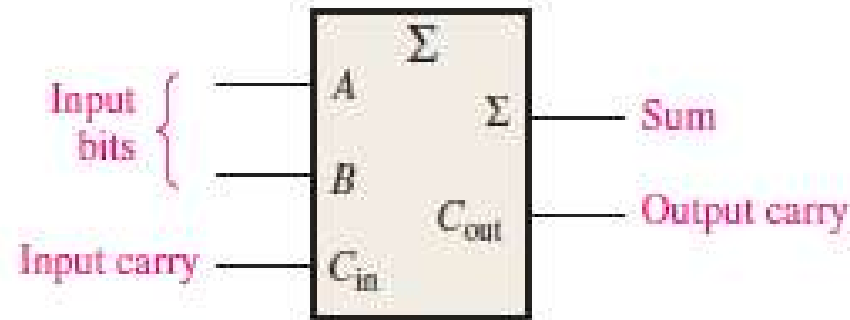- The full-adder accepts two input bits and an input carry and generates a sum output and an output carry.



The Full-Adder

Full-adder truth table.

A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C_{in} = input carry, sometimes designated as CI


C_{out} = output carry, sometimes designated as CO

Σ = sum


A and B = input variables (operands)

The Full-Adder Logic

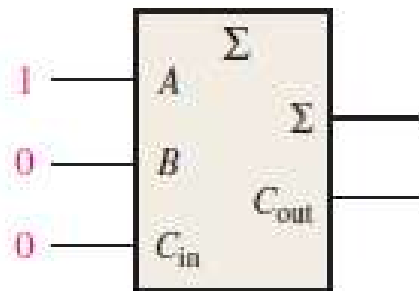
- For each of the three full-adders determine the outputs for the inputs shown.



(a)

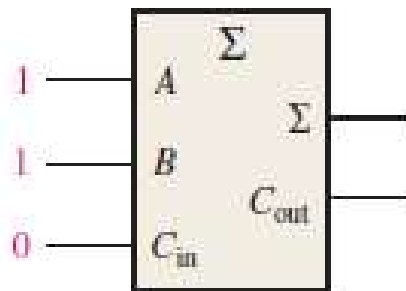

(b)

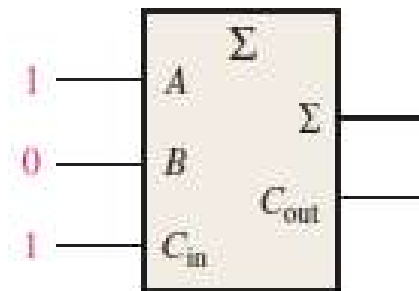

(c)

The Full-Adder Logic

- (a) The input bits are $A = 1$, $B = 0$, and $C_{in} = 0$.

$$1 + 0 + 0 = 1 \text{ with no carry}$$

Therefore, $\Sigma = 1$ and $C_{out} = 0$.

- (b) The input bits are $A = 1$, $B = 1$, and $C_{in} = 0$.

$$1 + 1 + 0 = 0 \text{ with a carry of } 1$$

Therefore, $\Sigma = 0$ and $C_{out} = 1$.

- (c) The input bits are $A = 1$, $B = 0$, and $C_{in} = 1$.

$$1 + 0 + 1 = 0 \text{ with a carry of } 1$$

Therefore, $\Sigma = 0$ and $C_{out} = 1$.